

3- ϕ Transformers

3 X 1- ϕ transformers can be connected on

- A-Y
- Y-D
- △-△
- Y-Y


to form 3- ϕ transformers.

A transformer with all 3- ϕ wound on the same core is preferred to 3X 1- ϕ transformers.

Consider: 3 X 1- ϕ each 25 MVA, 38.1 / 3.81 kV
For 3- ϕ Y-Y connected.

For the 3- ϕ transformer, rating: 75 MVA
66 / 6.6 kV

$$38.1 \sqrt{3} = 66$$

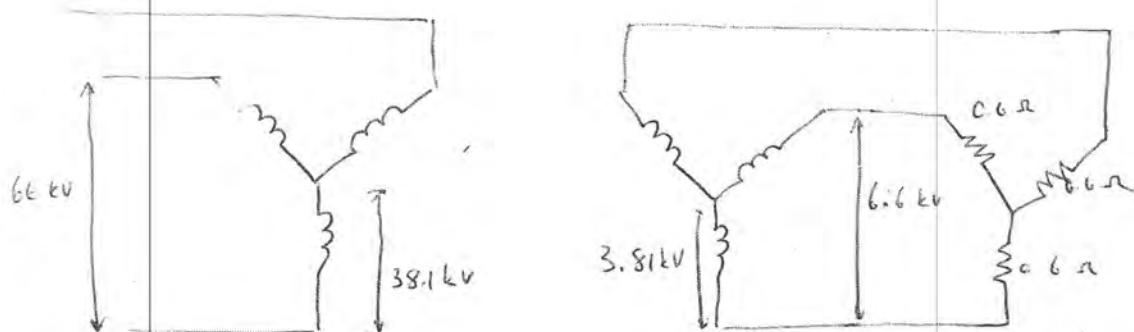


0.6 Ω /phase load is connected Y also.


Because the system is balanced, neutrals of the load and low-voltage side are at the same potentials.

$$\begin{aligned} Z_{l-n} & \text{ (measured from the high-tension side)} \\ &= 0.6 \left(\frac{66}{6.6} \right)^2 = 60 \Omega \end{aligned}$$

Other connection:

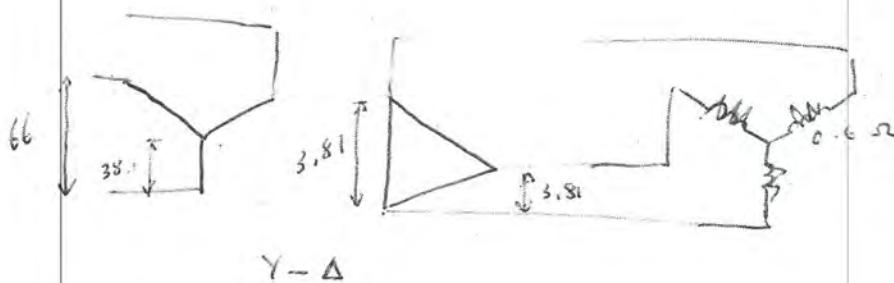

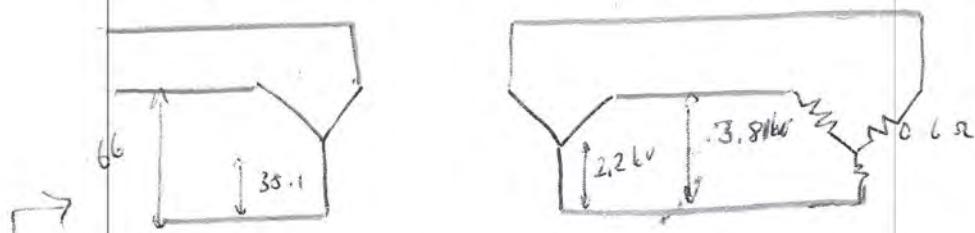This connection and the following give the same output voltage magnitude (there is a phase shift)



$$Z_L' = 0.6 \cdot \left(\frac{38.1}{2.2} \right)^2 = 0.6 \left(\frac{66}{3.81} \right)^2 = 180 \Omega$$

↓
square of the ratio of the l-l voltages,
not the square of the # of turns of each
winding.

→ M. 3-φ circuits

$$\frac{V_{B1}}{V_{B2}} = \frac{V_{LL-1}}{V_{LL-2}} \quad \text{regardless of the connection.}$$

Example $3 \times 1 - \delta$ transformer. rated 25 MVA, 38.1 / 31.81 kV
 Y-Δ connected.
 0.6 p.u./phase load. (Y)

Choose $S_B = 75 \text{ MVA}$

$V_B = 66 \text{ kV}$ for high-tension side


Find R_L^{pu} on the basis for low-tension side

Determine R_L referred to high-tension side


and p.u. value of this resistance

Solution:

Reactances

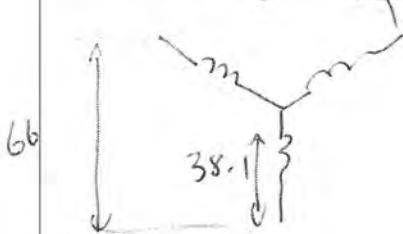

75 MVA

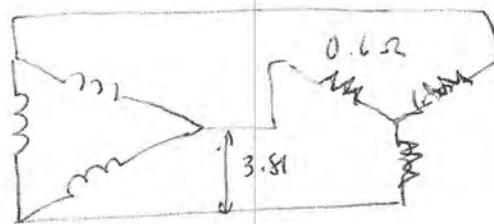

$$V_B = 3.81 \text{ kV}$$

$$Z_B = \frac{(3.81 \cdot 10^3)^2}{75 \cdot 10^6} = 0.1935 \Omega$$

$$R_L^{\text{pu}} = \frac{0.6}{0.1935} = 3.1 \text{ p.u}$$

$$Z_B = \frac{(66 \Omega)^2}{75} = 58.1 \Omega$$

$$R_L' = 0.6 * \left(\frac{66}{3.81}\right)^2 = 180 \Omega$$

$$R_L^{1, \text{pu}} = \frac{180}{38.1} = 3.10 \text{ p.u}$$



\Rightarrow p.u. value of impedances (R, X) are the same whether they are reflected to high or low tension sides.

Bad Example

(118)

Example:

X X

3- ϕ -transformer

400 MVA, 220 Y/220 kV

Short-circuit impedance measured ~~for~~ on the low-voltage side : 0.121 ω

This is a low-value \Rightarrow it can be considered leakage reactance.

? ~~per-unit~~ reactance of transformer

? the value to be used to represent this transformer in a system whose base on the high-tension side of the transformer is 100 MVA, 230 kV

Solution:


transformer reactance

$$\text{or } \text{its own base} = \frac{0.121}{\frac{(22)^2}{400}} = 0.1 \text{ p.u.}$$

$$\text{On the chosen base: } 0.1 * \left(\frac{220}{230}\right)^2 \frac{100}{400} = 0.0228 \text{ p.u.}$$


$\left[\begin{array}{l} 0.1 * \left(\frac{22}{400}\right)^2 \text{ don't give the} \\ \left(\frac{220}{230}\right)^2 \text{ same value} \\ \left(\frac{220^2}{400}\right) \text{ must be used} \end{array} \right]$
reflected value?

Ideal Transformer

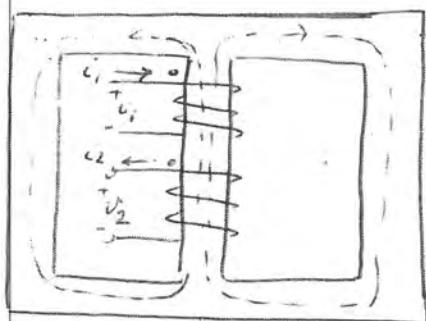

$N \rightarrow \infty$
flux: sinusoidal
 $R_{airgap} \rightarrow 0$
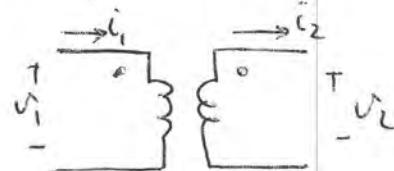
$$\left. \begin{array}{l} V_1 = e_1 = N_1 \frac{d\phi}{dt} \\ V_2 = e_2 = N_2 \frac{d\phi}{dt} \end{array} \right\} \Rightarrow \frac{V_1}{V_2} = \frac{N_1}{N_2}$$




Ampere's Law:

$$\oint \vec{H} \cdot d\vec{l} = i_{net} = N_1 i_1 - N_2 i_2 = 0 \quad (N \rightarrow \infty)$$

$$\Rightarrow N_1 I_1 = N_2 I_2$$
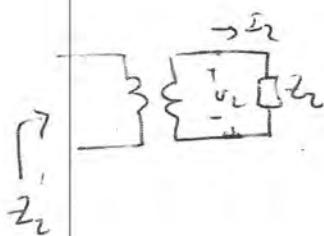
$$\Rightarrow \boxed{\frac{I_1}{I_2} = \frac{N_2}{N_1}}$$



$$V_2 = Z_2 I_2$$

$$\Rightarrow Z_2 = \frac{V_2}{I_2} = \frac{\frac{N_2}{N_1} V_1}{\frac{N_1}{N_2} I_1} = \left(\frac{N_2}{N_1} \right)^2 \frac{V_1}{I_1}$$

$$Z'_2 = \frac{V_1}{I_1} = \left(\frac{N_1}{N_2} \right)^2 Z_2$$

$$\text{Also. } V_1 I_1 = \frac{N_1}{N_2} V_2 \times \frac{N_2}{N_1} I_2 = V_2 I_2$$

$$\text{Similarly } V_1 I_1^* = V_2 I_2^* \text{ for ideal transformer}$$

Example:

$$N_1 = 2000, N_2 = 500$$

$$V_1 = 1200 \angle 0^\circ \text{ V} \quad I_1 = 5 \angle -30^\circ$$

$$Z_2, Z_2', V_2, I_2 = ?$$

$$V_2 = \frac{N_2}{N_1} V_1 = \frac{500}{2000} 1200 = 300 \angle 0^\circ$$

$$V_2 = \frac{N_2}{N_1} V_1 = \frac{500}{2000} 1200 = 300 \angle 0^\circ$$

$$I_2 = \frac{N_1}{N_2} I_1 = \frac{2000}{500} 5 \angle -30^\circ = 20 \angle -30^\circ$$

$$\Rightarrow Z_2 = \frac{V_2}{I_2} = \frac{300 \angle 0^\circ}{20 \angle -30^\circ} = 15 \angle 30^\circ \Omega$$

$$Z_2' = \left(\frac{N_1}{N_2}\right)^2 Z_2 = 16 Z_2 = 240 \angle 30^\circ \Omega$$

Equivalent circuit of a practical transformer

✓ is not infinite

winding resistance is zero
core losses ~~zero~~

leakage flux

when the secondary winding is open, primary current is not zero. A small current, called "magnetizing current" flows in primary.


iron losses : hysteresis losses

eddy-current losses \rightarrow thin laminated sheets of steel


∴ Magnetizing current is a highly inductive current.

energy loss in the core

(111)

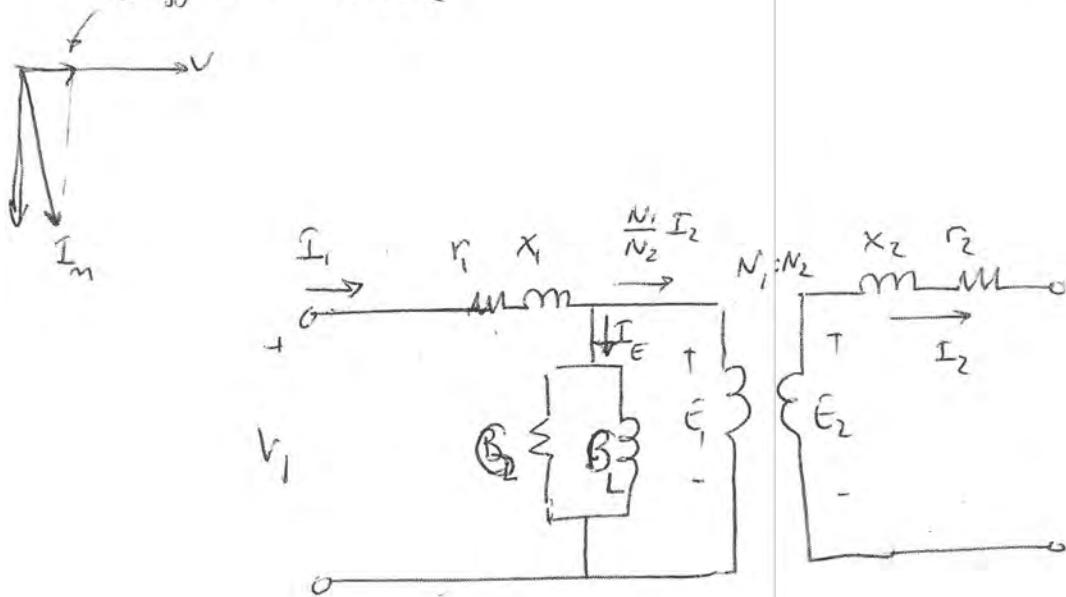

referred to high voltage side.

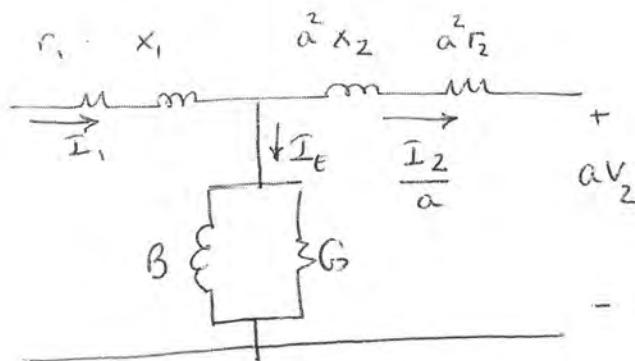


X = leakage reactance

$$a = \frac{N_1}{N_2}$$

I_E is usually ignored.

$$\Rightarrow R_i = R_1 + a^2 r_2$$

$$X_i = X_1 + a^2 X_2$$

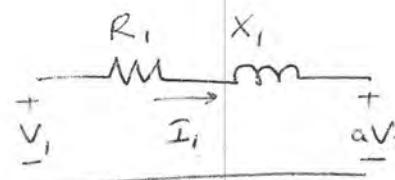

Example: 1- of transformer.

$$N_1 = 2000, N_2 = 500$$

$$r_1 = 2 \Omega, r_2 = 0.125 \Omega$$

$$x_1 = 8 \Omega, x_2 = 0.5 \Omega$$

$$z_2 = 12 \Omega, V_1 = 1200 V$$

$V_2 = ?$ no leakage regulation = ? reflect I_E .


Solution:

$$a = \frac{N_1}{N_2} = 4$$

$$R_i = r_1 + a^2 r_2 = 2 + 16 \times 0.125 = 4 \Omega$$

$$X_i = 8 + 16 \times 0.5 = 16 \Omega$$
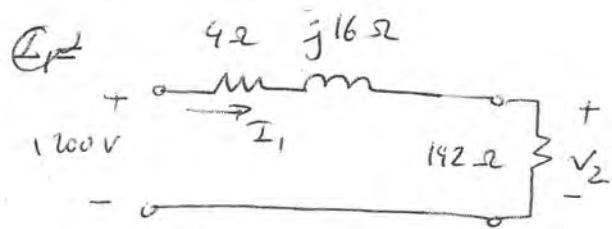
$$z'_2 = 16 \times z_2 = 16 \times 12 = 192 \Omega$$



$$I_1 = \frac{1200}{4 + 192 + j16} = 6.10 \angle -4.67^\circ$$

$$\alpha V_2 = 192 I_1 = 1171.6 \angle -4.67^\circ$$

$$V_2 = \frac{1171.6}{4} \angle -4.67^\circ = 292.9 \angle -4.67^\circ \text{ V}$$

voltage regulation : $\frac{\frac{1200}{4} - 292.9}{292.9} = 0.0242$
2.42 %

$G + jB_2$ can be measured by using open-circuit test.

$R + jX$ " " " short-circuit test

Per-Unit Impedances in Single-Phase Transformer Circuits

S_B = kVA rating of the transformer.

V_B { low voltage side value; if the parameters
are referred to low voltage
high voltage side value; if the parameters
are referred to high

per-unit impedance is the same


Example 1 ϕ transformer, 110/440 V, 2.5 kVA
Leakage reactance measured from the low-tension
side = 0.06 Ω \Rightarrow leakage reactance in pu.

$$S_B = 2.5 \times 10^3 \quad \left\{ \begin{array}{l} Z_B = \frac{V_B^2}{S_B} = \frac{(110)^2}{2.5 \times 10^3} = 4.84 \Omega \\ V_B = 110 \text{ V} \end{array} \right.$$

$$\Rightarrow X_{pu} = \frac{0.06}{4.84} = 0.0124 \text{ pu}$$

circuits
If many ~~transformers~~ are connected in through
transformers, different voltage bases are chosen for
each part. Voltage base is calculated by using
turns ratios. Same VA base is used for each
part.

example:

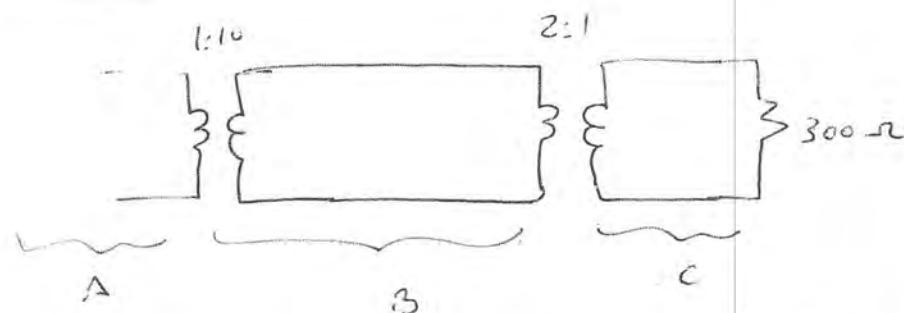

A-B transformer. 10000 kVA 138/13.8 kV leakage
reactance = 10%

B-C 10000 kVA 138/69 kV leakage
reactance 8%

Base in B is chosen 10000 kVA, 138 kV

find the pu. value of 300 ohm resistive load
referred to parts B and A.

Draw the impedance diagram neglecting magnetizing
current, transformer resistance and line impedances.

Determine the voltage regulation if the voltage at the
load is 66 kV with the assumption that the voltage
input to unit A remains constant.

$$\text{Solution: } V_B^A = 0.1 * V_B^B = 0.1 * 138 = 13.8 \text{ kV}$$

$$V_B^C = 0.5 * V_B^B = 0.5 * 138 = 69 \text{ kV}$$

$$Z_B^C = \frac{(V_B^C)^2}{S_B} = \frac{(69 \cdot 10^3)^2}{10000 \cdot 10^3} = 476.1 \text{ ohm}$$

$$\Rightarrow X^C = \frac{300}{476.1} = 0.63 \text{ pu}$$

$$Z_B^B = \frac{(V_B^B)^2}{S_B} = \frac{(138 \cdot 10^3)^2}{10 \cdot 10^6} = 1904 \Omega$$

(114)

$$X_B^B =$$


Load impedance referred to B: ~~300~~ $300 \times 2^2 = 1200 \Omega$

$$\Rightarrow X^B = \frac{1200}{1904} = 0.63 \text{ pu} \quad (\text{same})$$

$$Z_B^A = \frac{(V_B^A)^2}{S_B} = \frac{(138 \cdot 10^3)^2}{10 \cdot 10^6} = 19 \Omega$$

Load imp referred to A: $300 \times 2^2 \times (0.1)^2 = 12 \Omega$
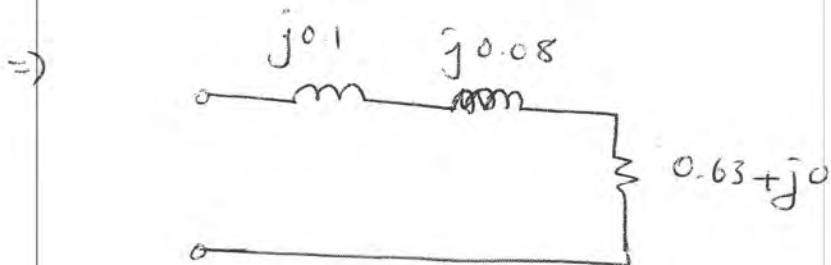
$$X^A = \frac{12}{19} = 0.63 \text{ pu.}$$



Voltage at load: $\frac{36 \text{ kV}}{69 \text{ kV}} = 0.957 \text{ pu.}$

Load current: $\frac{0.957}{0.63} = 1.52 \text{ pu.}$

Input voltage
~~Input voltage~~ = $(1.52) * \underline{\text{?}} + j(0.1 + 0.08) + 0.957$
 (Voltage at load
 with
 load removed) $= 0.957 + j0.274 \rightarrow 0.995 \text{ pu.}$

$$\Rightarrow r = \frac{0.995 - 0.957}{0.957} = 0.0397 \quad (3.97\%)$$

ONE-LINE DIAGRAM.

Standard symbols:



Attnote Fig. 6.25 / p 156 (Stevenson)

(Fig 10.1, page 493 of Chapman)

One-line diagram supplies the significant information about the system.

- Parameters are not shown
- $3\text{-}\phi \rightarrow 1\text{-}\phi$ (Balanced system)
- Amount of information depends on the purpose.
Circuit breakers may be omitted if local study is important.




Ground point is important to calculate unsymmetrical fault currents.

Most transformer neutrals are solidly grounded.


Generator neutrals are usually grounded through very large resistors (sometimes inductance coils)

A very simple power system:

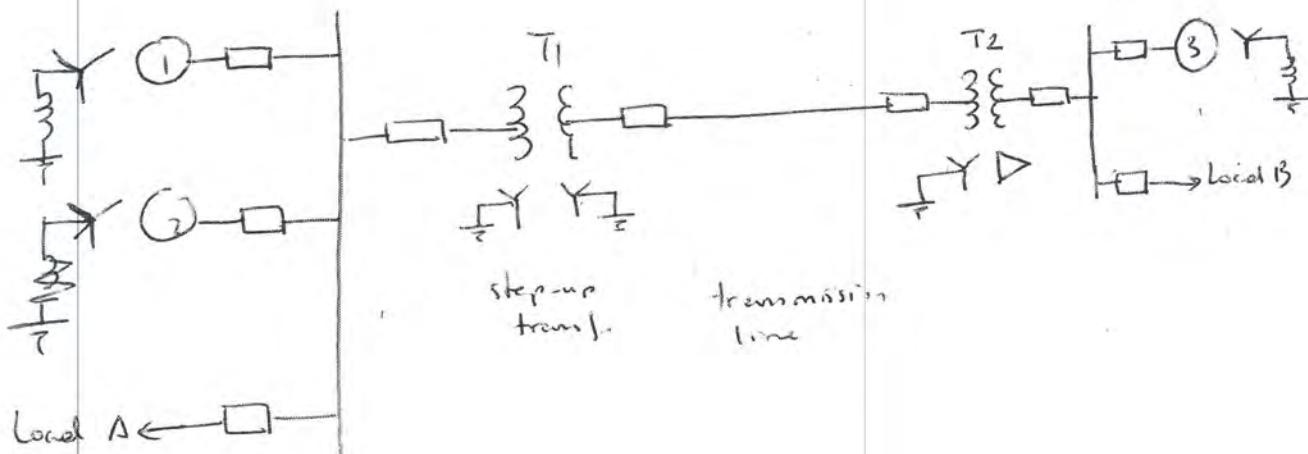

Network Calculations

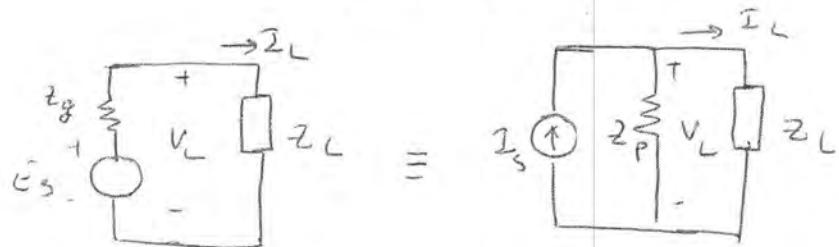constant emf = constant current source in parallel with impedance



$$V_L = E_g - Z_g I_L \quad = \quad V_L = (I_s - I_L) Z_p \\ = Z_p I_s - Z_p I_L$$

$$\Rightarrow E_g - Z_g I_L = Z_p I_s - Z_p I_L$$


$$Z_p = Z_g \rightarrow Z_p I_s = E_g \\ \Rightarrow I_s = E_g / Z_p$$

Same can be done for active loads

Node Equations


if more than two components are connected to a node, it is called "major node".

a sample one-line diagram:

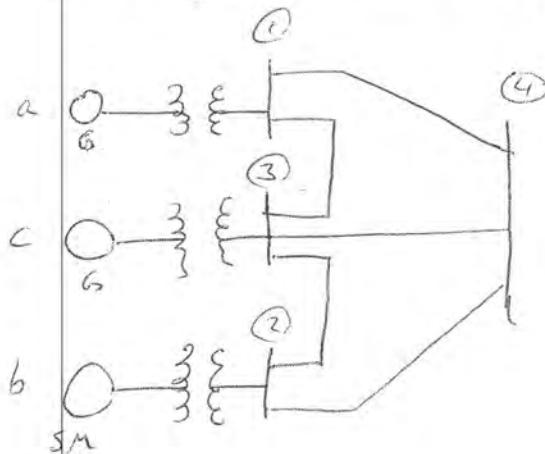


Reactive diagram -

(126)

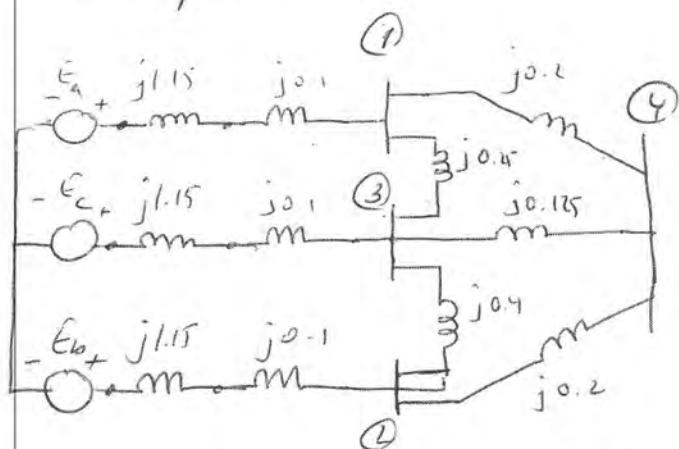

$E \rightarrow$ replaced by I
 $I \rightarrow$ replaced by Y
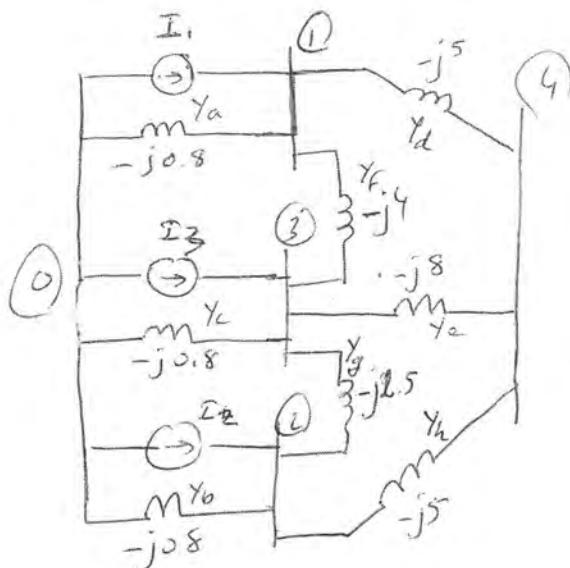
$$\frac{1}{j(1.15+0.1)} = \frac{1}{j1.25} = 0.8(-j)$$



KCL (Node 1) $I_1 = Y_a V_1 + Y_f (V_1 - V_3) + Y_d (V_1 - V_4)$

(Node 4) $0 = Y_d (V_4 - V_1) + Y_h (V_4 - V_2) + Y_e (V_4 - V_3)$

$$\Rightarrow I_1 = V_1 [Y_a + Y_f + Y_d] - V_3 Y_f - V_4 Y_d$$

$$0 = -V_1 Y_d - V_2 Y_h - V_3 Y_e + V_4 (Y_d + Y_e + Y_h)$$

Same can be written for each node.

A matrix form set of equations is obtained.

The solution yields the currents when

V_1, V_2, V_3, V_4 are known

(127)

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \underbrace{\begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & Y_{14} \\ Y_{21} & Y_{22} & Y_{23} & Y_{24} \\ Y_{31} & Y_{32} & Y_{33} & Y_{34} \\ Y_{41} & Y_{42} & Y_{43} & Y_{44} \end{bmatrix}}_{Y_{bus}} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

Y_{ij}
i: the node at which the
 current is expressed
 effect cause
j: the voltage that causes
 that component of current

Y_{bus} : bus admittance matrix
 * - symmetrical

Y_{ii} : self admittances (desv. point adm.)
 others mutual admittances (transfer adm.)

for a network with N independent nodes

$$I_k = \sum_{n=1}^N Y_{kn} V_n$$

Example: $E_A = 1.5 \angle 0^\circ$
 $E_B = 1.5 \angle -36.87^\circ$
 $E_C = 1.5 \angle 0^\circ$

$$\Rightarrow I_1 = I_3 = \frac{1.5 \angle 0^\circ}{j1.25} = 1.2 \angle -90^\circ = -j1.2 \text{ p.u.}$$

$$I_2 = \frac{1.5 \angle -36.87^\circ}{j1.25} = 1.2 \angle -126.87^\circ = -0.72 - j0.96 \text{ p.u.}$$

self adm.

$$Y_{11} = -j0.8 - j4 - j5 = -j9.8$$

$$Y_{22} = -j0.8 - j2.5 - j5 = -j8.3$$

$$Y_{33} = -j4 - j0.8 - j2.5 = -j7.3$$

$$Y_{44} = -j5 - j8 - j5 = -j18$$

$$Y_{12} = Y_{21} = 0$$

$$Y_{13} = Y_{31} = +j4$$

$$Y_{14} = Y_{41} = +j5$$

$$Y_{23} = Y_{32} = -j2.5$$

$$Y_{24} = Y_{42} = +j5$$

$$Y_{34} = Y_{43} = +j8$$

\Rightarrow

$$\begin{bmatrix} 0-j1.2 \\ -0.72-j0.96 \\ 0-j1.2 \\ 0 \end{bmatrix} = \underbrace{\begin{bmatrix} -j9.8 & j0 & j4 & j5 \\ j0 & -j8.3 & j2.5 & j5 \\ j4 & j2.5 & -j15.3 & j8 \\ j5 & +j5 & j8 & -j18 \end{bmatrix}}_{Y_{bus}} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

Y_{bus}

$$Y_{bus}^{-1} \begin{bmatrix} -j1.2 \\ -0.72-j0.96 \\ -j1.2 \\ 0 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} 1.4111-j0.2668 \\ 1.3830-j0.3508 \\ 1.4059-j0.2824 \\ 1.4009-j0.2971 \end{bmatrix}$$

$$\Rightarrow V_1 = 1.436 \angle -10.71^\circ$$

$$V_2 = 1.427 \angle -14.24^\circ$$

$$V_3 = 1.434 \angle -11.36^\circ$$

$$V_4 = 1.432 \angle -11.97^\circ$$

$$Y_{bus}^{-1} = Z_{bus}^{-1} = \begin{bmatrix} j0.4774 & j0.3706 & j0.4020 & j0.4142 \\ j0.3706 & j0.4872 & j0.3922 & j0.4126 \\ j0.4020 & j0.3922 & j0.4558 & j0.4232 \\ j0.4142 & j0.4126 & j0.4232 & j0.4733 \end{bmatrix}$$

Matrix Partitioning

(129)

$$A = \begin{bmatrix} a_{11} & a_{12} & | & a_{13} \\ a_{21} & a_{22} & | & a_{23} \\ a_{31} & a_{32} & | & a_{33} \end{bmatrix} = \begin{bmatrix} D & E \\ F & G \end{bmatrix}$$

$$D = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \quad E = \begin{bmatrix} a_{13} \\ a_{23} \end{bmatrix}$$

$$F = \begin{bmatrix} a_{31} & a_{32} \end{bmatrix} \quad G = a_{33}$$

if $A B = C$ where

$$B = \begin{bmatrix} b_{11} \\ b_{21} \\ b_{31} \end{bmatrix} = \begin{bmatrix} H \\ J \end{bmatrix}$$

$$\Rightarrow C = \begin{bmatrix} D & E \\ F & G \end{bmatrix} \begin{bmatrix} H \\ J \end{bmatrix} = \begin{bmatrix} DH + EJ \\ FH + GJ \end{bmatrix} = \begin{bmatrix} M \\ N \end{bmatrix}$$

$$\text{where } M = DH + EJ$$

$$N = FH + GJ$$

$$N = \begin{bmatrix} a_{31} & a_{32} \end{bmatrix} \begin{bmatrix} b_{11} \\ b_{21} \end{bmatrix} + a_{33} b_{31}$$

$$= a_{31} b_{11} + a_{32} b_{21} + a_{33} b_{31}$$

⚠ row-column dimensions must be properly chosen.

Node Elimination by Matrix Algebra

(130)

Nodes at which current doesn't enter or leave the network, can be eliminated.

$$I = Y_{bus} V$$

Nodes to be eliminated are put to lower rows of the matrices.

$$\begin{bmatrix} I_A \\ I_X \end{bmatrix} = \begin{bmatrix} K & L \\ L^T & M \end{bmatrix} \begin{bmatrix} V_A \\ V_X \end{bmatrix}$$

I_X : Matrices of nodes to be eliminated

$$V_X \quad [I_X \rightarrow 0]$$

$$I_A = KV_A + LV_X$$

$$I_X = L^T V_A + MV_X \Rightarrow -L^T V_A = MV_X$$


$$-M^{-1} L^T V_A = V_X$$

$$\Rightarrow I_A = KV_A + L \left[-M^{-1} L^T V_A \right]$$

$$= \underbrace{[K - LM^{-1}L^T]}_{Y_{bus}} V_A$$

$$Y_{bus}$$

Example: G and T are removed from bus 3

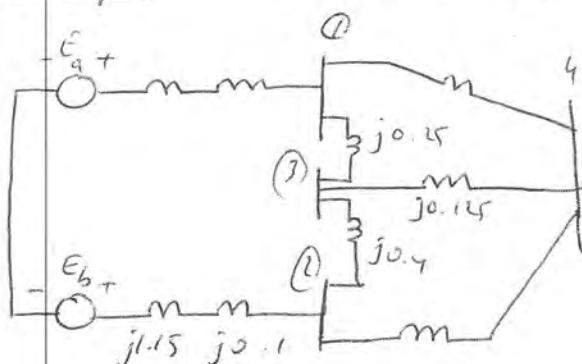

Eliminate node 3, 4

$$Y_{bus} = \begin{bmatrix} -j9.8 & 0 & j4 & j5 \\ 0 & -j8.3 & j2.5 & j5 \\ j4 & j2.5 & -j14.5 & j8 \\ j5 & j5 & j8 & -j18 \end{bmatrix} = \begin{bmatrix} K & L \\ LT & M \end{bmatrix} \quad (131)$$

$$M = \begin{bmatrix} -j14.5 & j8 \\ j8 & -j18 \end{bmatrix}$$

$$\det M = -14.5 \cdot 18 + 64 = -197$$

$$M^{-1} = \frac{1}{-197} \begin{bmatrix} -j18 & -j8 \\ -j8 & -j14.5 \end{bmatrix} = \begin{bmatrix} j0.0914 & j0.0406 \\ j0.0406 & j0.0736 \end{bmatrix}$$

$$LM^{-1}L^T = \begin{bmatrix} j4 & j5 \\ j2.5 & j5 \end{bmatrix} \begin{bmatrix} j0.0914 & j0.0406 \\ j0.0406 & j0.0736 \end{bmatrix} \begin{bmatrix} j4 & j2.5 \\ j5 & j5 \end{bmatrix}$$


$$= - \begin{bmatrix} j4.9264 & j4.0736 \\ j4.0736 & j3.4264 \end{bmatrix}$$

$$Y_{bus} = K - LM^{-1}L^T = \begin{bmatrix} -j4.8736 & j4.0736 \\ j4.0736 & -j4.8736 \end{bmatrix}$$

\Rightarrow admittance between 1 and 2 : $-j4.8736$
 $-j4.0736$

p.u. impedance between 1 & 2 $j\frac{1}{4.0736}$

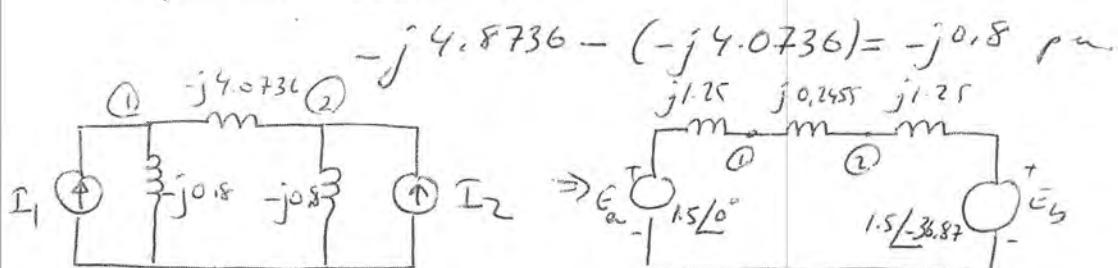admittance between each of these nodes and reference node :



$$I = \frac{E_a - E_b}{j(1.25 + 1.25 + 0.2455)} = \frac{1.5 - 1.5 \angle -36.87^\circ}{j 2.7455} \quad (132)$$

$$= 0.3278 - j 0.1093 = 0.3455 \angle -18.44^\circ \text{ pu}$$

Power out of source a is:

$$1.5 \angle 0^\circ + 0.3455 \angle 18.44^\circ = 0.492 + j 0.164 \text{ pu}$$

Power into source b:

$$1.5 \angle -36.87^\circ + 0.3455 \angle 18.44^\circ = 0.492 - j 0.164 \text{ pu.}$$

Note: Reactive VA values are equal.

$$(0.3455)^2 2.7455 = 0.328 = 0.164 + j 0.164$$

The voltage at node 1:

$$1.50 \angle 0^\circ - j 1.25 + 0.3455 \angle -18.44^\circ$$

$$= 1.363 - j 0.41 \text{ pu}$$

Node elimination is very important for high ~~s~~ when the number of nodes is high. Then, matrix inversion which is very complicated, becomes avoided.

Elimination: One node at a time, start from the highest node number.

$$Y_{bus} = \left\{ \begin{array}{c|c} \overbrace{\begin{matrix} Y_{11} & Y_{12} & \cdots & Y_{1j} & \cdots & Y_{1n} \\ Y_{21} & Y_{22} & \cdots & Y_{2j} & \cdots & Y_{2n} \\ \vdots & & & & & \\ Y_{n1} & Y_{n2} & \cdots & Y_{nj} & \cdots & Y_{nn} \end{matrix}}^k & | \\ \hline \underbrace{\begin{matrix} Y_{11} & Y_{12} & \cdots & Y_{1j} & \cdots & Y_{1n} \\ Y_{21} & Y_{22} & \cdots & Y_{2j} & \cdots & Y_{2n} \\ \vdots & & & & & \\ Y_{n1} & Y_{n2} & \cdots & Y_{nj} & \cdots & Y_{nn} \end{matrix}}_m & | \end{array} \right\} y$$

$$\Rightarrow Y_{bus} = \begin{bmatrix} Y_{11} & \cdots & Y_{1j} & Y_{1,n+1} \\ \vdots & & & \\ Y_{n1} & \cdots & Y_{nj} & \cdots & Y_{n,n+1} \end{bmatrix} - \frac{1}{Y_{nn}} \begin{bmatrix} Y_{1j} \\ Y_{2j} \\ \vdots \\ Y_{nj} \end{bmatrix} \begin{bmatrix} Y_{11} & Y_{1j} & \cdots & Y_{1,n+1} \\ Y_{21} & Y_{22} & \cdots & Y_{2,n+1} \\ \vdots & & & \\ Y_{n1} & Y_{n2} & \cdots & Y_{n,n+1} \end{bmatrix}$$

$$\Rightarrow Y_{kj(\text{new})} = Y_{kj(\text{orig})} - \frac{Y_{kn} Y_{nj}}{Y_{nn}}$$

Example:

$$Y_{bus} = \begin{bmatrix} -j9.8 & 0 & j4.0 & j5.0 \\ 0 & -j8.3 & j2.5 & j5.0 \\ j4.0 & j2.5 & -j14.5 & j8.0 \\ -j5 & j5 & j8 & -j18 \end{bmatrix}$$

First remove node 4. ($n=4$)

$$Y_{31(\text{new})} = Y_{31(\text{orig})} - \frac{Y_{34} Y_{41}}{Y_{44}} = j4 - \frac{j5 \times j8}{-j18} = j(4 + \frac{40}{18}) = j6.22$$

$$Y_{32}^{\text{new}} = j2.5 - \frac{j5 \times j8}{-j18} = j4.72$$

$$Y_{33}^{\text{new}} = -j14.5 - \frac{j8 \times j8}{-j18} = -j10.94$$

$$Y_{21}^{\text{new}} = 0 - \frac{j5 \times j5}{-j18} = j1.3889$$

$$Y_{22}^{\text{new}} = -j8.3 - \frac{j5 \times j5}{-j18} = -j6.91$$

$$Y_{23}^{\text{new}} = j2.5 - \frac{j8 \times j5}{-j18} = j4.72$$

$$Y_{11}^{\text{new}} = -j9.8 - \frac{j5 \times j5}{-j18} = -j8.41$$

$$Y_{12}^{\text{new}} = 0 - j \frac{5 \times j5}{-j18} = j1.3889$$

$$Y_{13}^{\text{new}} = j4 - j \frac{8 \times j5}{-j18} = \cancel{j17.78} j6.22$$

$$\Rightarrow Y_{\text{bus}} = \begin{bmatrix} -j8.41 & j2.3889 & j4.72 \\ j1.3889 & -j6.91 & j4.72 \\ \cancel{j6.22} & j4.72 & -j10.94 \end{bmatrix}$$

Eliminate node 3.

$$\Rightarrow Y_{\text{bus}} = \begin{bmatrix} -j4.87 & j4.072 \\ j4.072 & -j4.87 \end{bmatrix}$$

Bus Admittance and Impedance Matrix


(135)

$$Z_{bus} = Y_{bus}^{-1}$$

$$Z_{bus} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix}$$

For a
3-node system
(3 independent)

$$I = Y_{bus} V$$

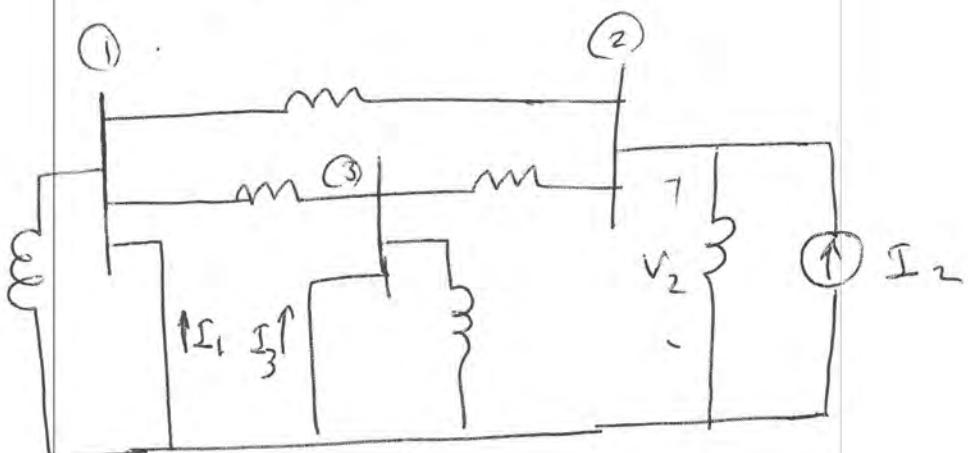

For a 3-node system:

$$I_2 = Y_{21} V_1 + Y_{22} V_2 + Y_{23} V_3$$

If $V_1 = V_3 = 0$ (short nodes 1 and 3)
inject I_2 to node 2

$$\Rightarrow I_2 = Y_{22} V_2$$

$$Y_{22} = \frac{I_2}{V_2}$$

$$V_1 = V_3 = 0$$

\rightarrow Y_{22} = current leaving the node
node voltage

The resultant admittance is the negative of the admittance directly connected between nodes 1 and 2

$$Y_{12} = -Y_{bus}$$

$$I = Y_{bus} V$$

$$Y_{bus}^{-1} \cdot I = Z_{bus} I = V$$


V and I are column ~~vectors~~ matrices of the node voltages and currents entering the nodes from current sources.

$$V_1 = Z_{11} I_1 + Z_{12} I_2 + Z_{13} I_3$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 + Z_{23} I_3$$

$$V_3 = Z_{31} I_1 + Z_{32} I_2 + Z_{33} I_3$$

$$Z_{22} = \frac{V_2}{I_2} \quad \left| \begin{array}{l} I_1 = I_3 = 0 \\ \text{open current sources} \\ 1 \text{ and } 3, \text{ inject } I_2 \text{ to } ② \\ \text{apply } V_2 \text{ to node } ② \end{array} \right.$$

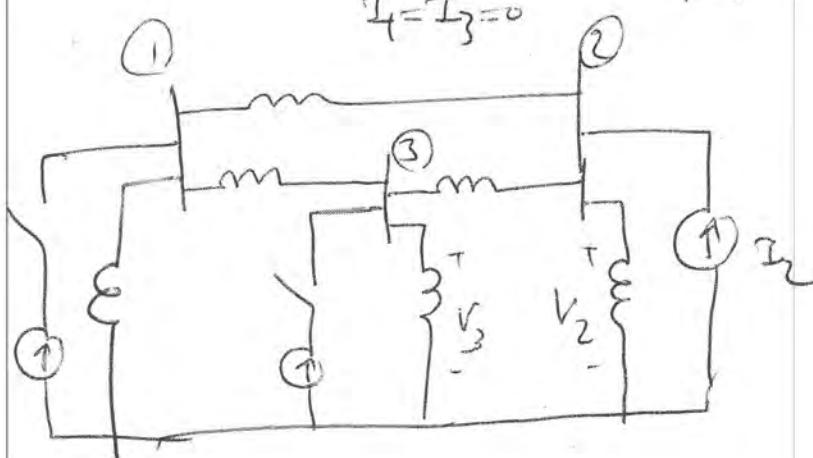

transfer impedances

also.


$$Z_{12} = \frac{V_1}{I_2} \quad | \\ I_1 = I_3 = 0$$

(137)

$$Z_{32} = \frac{V_3}{I_2} \quad | \\ I_1 = I_3 = 0$$

Example

$$X_C = 5 \text{ p.u}$$

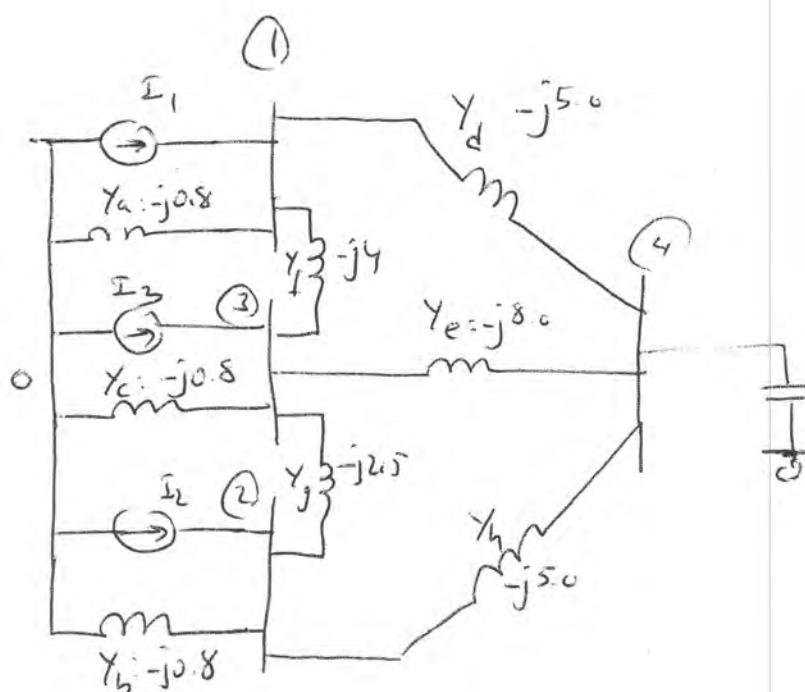


Find the current drawn by the capacitor

Solution: System before the cap was connected :

$$E_{th} = 1.432 \angle -11.97^\circ \text{ Thevenin volt.}$$

Thevenin imp. ?

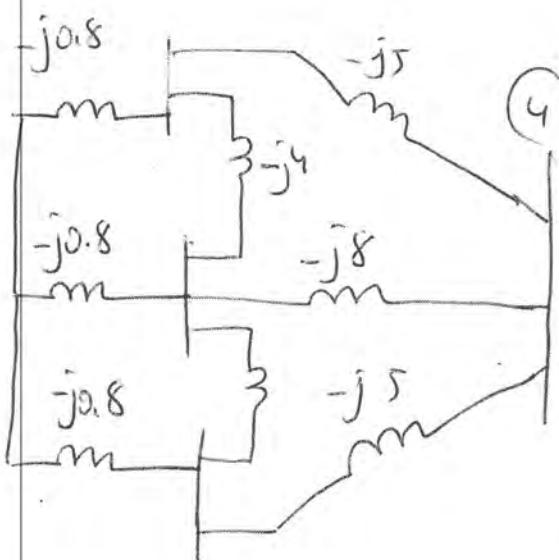

$$V_4 = Z_{41} I_1 + Z_{42} I_2 + Z_{43} I_3 + Z_{44} I_4$$

$$I_1 = I_2 = I_3 = 0$$

$$\Rightarrow Z_{41} = Z_{44} = j0.4733 \quad (\text{calculated before})$$

current drawn by the cap.

$$\Rightarrow I_C = \frac{1.432 / -11.97^\circ}{j0.4733 - j5} = 0.316 / 78.03^\circ \text{ p.u.}$$

Example (Cont'd)

a current of $-0.316 / 78.03^\circ$ p.u.

is injected to (4). Find the voltages of (1), (2), (3), (4)

Solution: Node voltages before injection are already known. We need to know the effect of this injected current alone. So, short all emf's, and calculate $Z_{14}, Z_{24}, Z_{34}, Z_{44}$; i.e. the parameters for this node.

(139)

$$V_1 = Z_{14} I_4 = j0.4142 * (-0.316) \angle 78.03^\circ \\ = 0.1309 \angle -11.97^\circ$$

$$V_2 = Z_{24} I_4 = 0.1304 \angle -11.97^\circ$$

$$V_3 = Z_{34} I_4 = 0.1337 \angle -11.97^\circ$$

$$V_4 = Z_{44} I_4 = 0.1496 \angle -11.97^\circ$$

By superposition,

$$V_1 = 1.436 \angle -10.71^\circ + 0.1309 \angle -11.97^\circ = 1.567 \angle -10.81^\circ$$

$$V_2 = 1.427 \angle -14.24^\circ + 0.1304 \angle -11.97^\circ = 1.557 \angle -14.04^\circ$$

$$V_3 = 1.434 \angle -11.36^\circ + 0.1337 \angle -11.97^\circ = 1.568 \angle -11.41^\circ$$

$$V_4 = 1.432 \angle -11.97^\circ + 0.1396 \angle -11.97^\circ = 1.582 \angle -11.97^\circ$$

if the network is considerably inductive,
then ZI may be added to existing voltages
without worrying about angles.

* A capacitive addition causes voltage increase in the line.

Modification of an existing Z_{bus} .

$$[Z_{orig}]_{n \times n}$$

Z_b will be added to Z_{bus} .

b, i, j, k : original

p : new bus

Case 1: Adding Z_b from a new bus P to reference bus through Z_b w/o any connection to other existing buses \rightarrow original bus voltages don't change. I_p is injected to new bus.


$$\Rightarrow V_p = I_p Z_b$$

$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ V_p \end{bmatrix} = \underbrace{\begin{bmatrix} Z_{orig} & \begin{bmatrix} 0 \\ 0 \\ \vdots \\ 0 \\ -I_p \end{bmatrix} \\ \hline 0 & \begin{bmatrix} Z_b \end{bmatrix} \end{bmatrix}}_{Z_{bus}(\text{new})} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_p \end{bmatrix}$$

(141)

Case 2 z_b : from p to existing k.

I_p is injected towards P

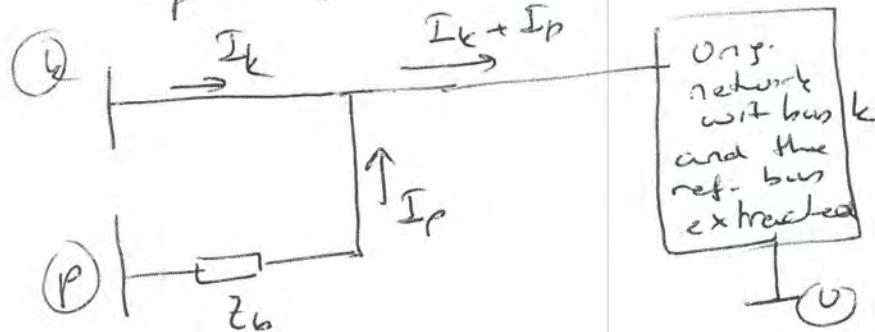

$$V_{k(\text{new})} = V_{k(\text{orig})} + I_p z_{kk}$$

$$V_p = V_{k(\text{orig})} + I_p z_{kk} + I_p z_b$$

$$= \underbrace{I_1 z_{k1} + I_2 z_{k2} + \dots + I_n z_{kn}}_{V_{k(\text{orig})}} + I_p (z_{kk} + z_b)$$

$V_{k(\text{orig})}$

$$\Rightarrow \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ V_p \end{bmatrix} = \begin{bmatrix} z_{\text{orig}} \\ z_{k1} & z_{k2} & \cdots & z_{kn} & z_{kk} + z_b \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_p \end{bmatrix}$$

Case 3

Add Z_b from bus k to ref. bus

- First ~~create~~ add a new bus p
- Then connect p to k through Z_b
- Then short p to ground $\Rightarrow V_p = 0$


$$\begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \\ V_{p=0} \end{bmatrix} = \begin{bmatrix} Z_{\text{only}} \\ Z_{ka} - Z_{k\alpha} \\ Z_{kk} + Z_b \\ Z_{kb} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ \vdots \\ I_n \\ I_p \end{bmatrix}$$

eliminate:

$$\Rightarrow Z_{hi(\text{new})} = Z_{hi(\text{only})} - \frac{Z_{h(n+1)} I_{(n+1)i}}{Z_{kk} + Z_b}$$

Case 4

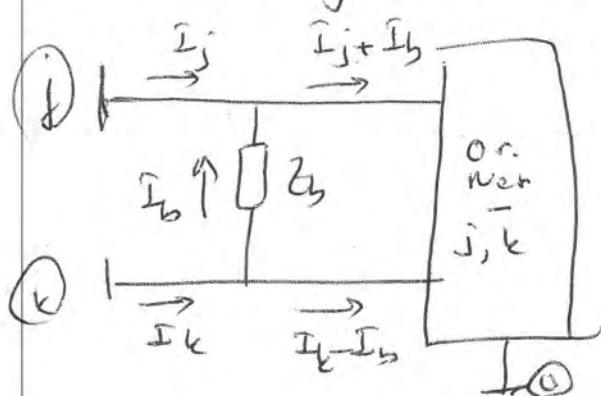Add Z_b between 2 existing buses j and k .



(143)

$$V_i = z_{ii} I_1 + \dots + z_{ij} (I_j + \bar{I}_b) + z_{ik} (I_k - \bar{I}_b) + \dots$$

$$\Rightarrow V_i = z_{ii} I_1 + \dots + z_{ij} I_j + z_{ik} I_k + \dots + \bar{I}_b (z_{ij} - z_{ik})$$

similarly :

$$V_j = z_{jj} I_1 + \dots + z_{jj} I_j + z_{jk} I_k + \dots + \bar{I}_b (z_{jj} - z_{jk})$$

$$V_k = z_{kk} I_1 + \dots + z_{kj} I_j + z_{kk} I_k + \dots + \bar{I}_b (z_{kj} - z_{kk})$$

we need one more eqn. (\bar{I}_b is unknown)

$$V_k - V_j = z_b \bar{I}_b$$

or

$$0 = z_b \bar{I}_b + V_j - V_k$$

$$\Rightarrow 0 = z_b \bar{I}_b + (z_{ji} - z_{ki}) I_1 + \dots + (z_{jj} - z_{kj}) I_j + (z_{jk} - z_{kk}) I_k + \dots + (z_{jj} + z_{kk} - 2z_{jk}) \bar{I}_b$$

$$\Rightarrow 0 = (z_{ji} - z_{ki}) I_1 + \dots + (z_{jj} - z_{kj}) I_j + (z_{jk} - z_{kk}) I_k + \dots + z_{bb} \bar{I}_b$$

where

$$z_{bb} = z_b + z_{jj} + z_{kk} - 2z_{jk}$$

 \Rightarrow


(144)

$$\begin{bmatrix} V_1 \\ \vdots \\ V_j \\ \vdots \\ V_k \\ \vdots \\ 0 \end{bmatrix} = \begin{bmatrix} Z_{00} \\ \vdots \\ Z_{jj} \\ \vdots \\ Z_{kk} \\ \vdots \\ Z_{nn} \end{bmatrix} - \frac{(Z_{ji} - Z_{ii}) \dots (Z_{jj} - Z_{ii}) \dots (Z_{kk} - Z_{ii})}{Z_{bb}} \begin{bmatrix} Z_{ii} - Z_{jj} \\ Z_{ii} - Z_{kk} \\ \vdots \\ Z_{ii} - Z_{nn} \\ Z_{ji} - Z_{kj} \\ Z_{ki} - Z_{kj} \\ \vdots \\ Z_{nj} - Z_{nk} \end{bmatrix} \begin{bmatrix} I_1 \\ \vdots \\ I_j \\ \vdots \\ I_k \\ \vdots \\ I_n \\ I_b \end{bmatrix}$$

eliminate $(n+1)^{th}$ row and column.

$$Z_{hi(\text{new})} = Z_{hi(\text{orig})} - \frac{Z_h(n+1) Z_{(n+1)i}}{Z_b + Z_{jj} + Z_{kk} - 2Z_{jk}}$$

Example:

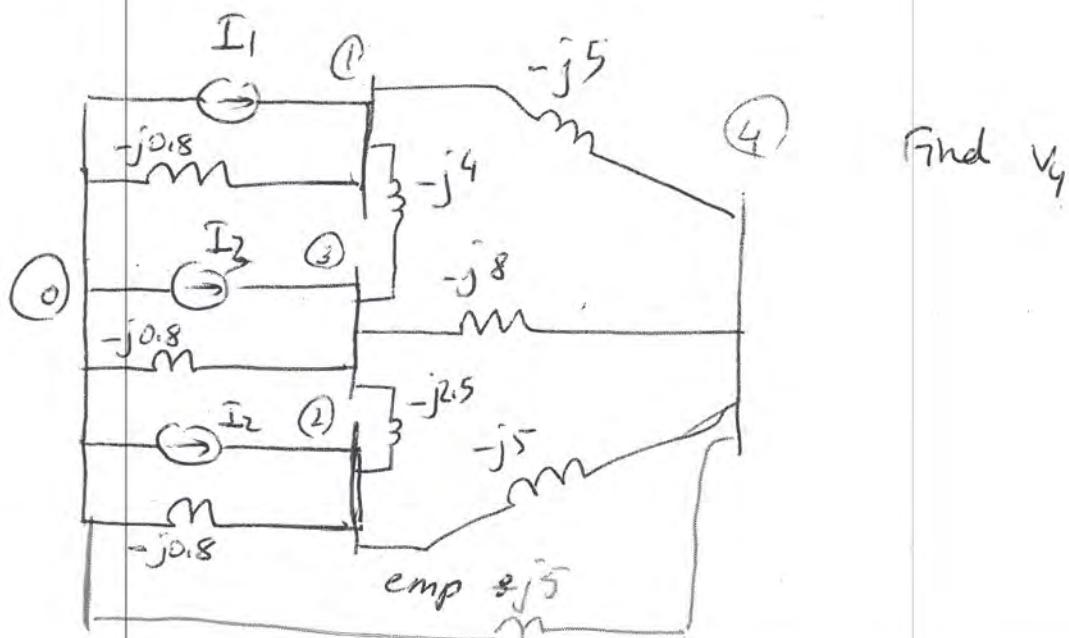

$$Z_b = -j5$$

(145)

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ j0.4142 \\ j0.4126 \\ j0.4232 \\ j0.4733 \end{bmatrix}$$

$$Z_{44} + Z_b = j0.4733 - j5 \\ = -j4.5267$$

Eliminate 5th row and column:

$$Z_{11} = j0.474 - \frac{j0.4142 * j0.4142}{-j4.5267} = j0.5153$$

Page 187


page 186

$$\Rightarrow V_4 = 1.5474 - j0.3281 = 1.582 \angle -11.97^\circ$$

Direct Determination of Z_{bus}


Obtaining Z_{bus} directly is easier than inverting Y_{bus} for large systems.

Start with one impedance

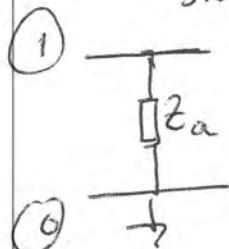


$$V_1 = I_1 Z_a \quad : \text{can be considered as a matrix eqn.}$$

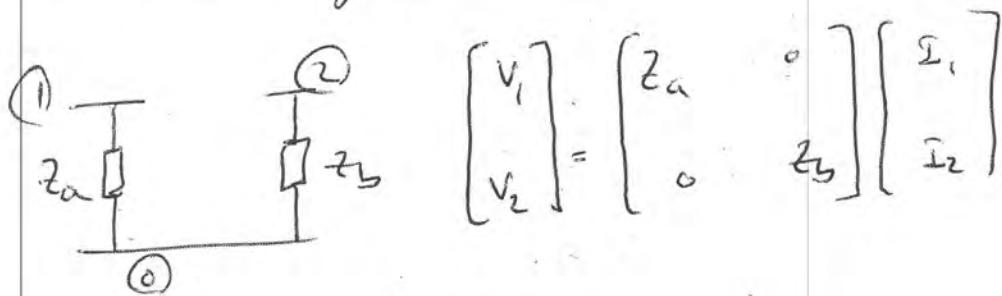Now connect Z_b between another bus and reference bus



Proceed accordingly

Example: $j0.3$

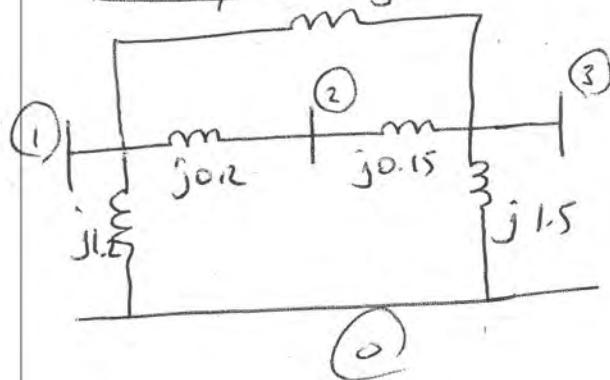

Start with ①

$$V_1 = j1.2 \quad I_1 \Rightarrow Z_{bus} = j1.2$$

Now, bus ② ($j0.2$ is connected between ① and ②)

$$Z_{bus(\text{new})} = \begin{bmatrix} j1.2 & j1.2 \\ j1.2 & j1.4 \end{bmatrix}$$

$\overset{z_{11}}{\uparrow}$
 $\underset{z_{11} + z_{22}}{\uparrow}$

Between ~~③~~ ③ and ① : $j0.3$

$$\Rightarrow Z_{bus(\text{new})} = \begin{bmatrix} j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.2 \\ j1.2 & j1.2 & j1.5 \end{bmatrix}$$

$\overset{z_{11}}{\uparrow}$
 $\overset{z_{21}}{\uparrow}$
 $\overset{z_{11} + z_{33}}{\uparrow}$

Now: $Z_b = j1.5$ between ③ and ① (case ③)

$$Z_{bus(\text{new})} = \begin{bmatrix} j1.2 & j1.2 & j1.2 & j1.2 \\ j1.2 & j1.4 & j1.2 & j1.2 \\ j1.2 & j1.2 & j1.5 & j1.5 \\ j1.2 & j1.2 & j1.5 & j1.5 \end{bmatrix}$$

Node ④
8
 $\rightarrow Z_{33} + Z_b$

$\overset{z_{11}}{\uparrow}$
 $\overset{z_{21}}{\uparrow}$
 $\overset{z_{31}}{\uparrow}$
 $\overset{z_{32}}{\uparrow}$
 $\overset{z_{33}}{\uparrow}$

Now, eliminate Row 4 and Column 4

jots between ② and ③ Case: 4



$$\underline{z_{11} = j^{1.2}}$$

$$z_{11} = z_{11(\text{orig})} - \frac{z_{14} \cdot z_{41}}{z_{44}}$$

$$= j^{1.2} - \frac{j^{1.2} \times j^{1.2}}{j^3} = j^{0.72}$$

$$z_{12} = z_{12(\text{orig})} - \frac{z_{14} z_{42}}{z_{44}}$$

$$= j^{1.2} - \frac{j^{1.2} \times j^{1.2}}{j^3} = j^{0.72}$$

$$z_{13} = j^{1.2} - \frac{j^{1.2} \times j^{1.5}}{j^{3.0}} = j^{0.6}$$

$$z_{22} = j^{1.4} - \frac{j^{1.2} \times j^{1.2}}{j^3} = j^{0.92}$$

$$z_{33} = j^{1.5} - \frac{j^{1.5} \times j^{1.5}}{j^3} = j^{0.75}$$

$$Z_{bus(new)} = \begin{bmatrix} j0.72 & j0.72 & j0.60 \\ j0.72 & j0.92 & j0.60 \\ j0.60 & j0.60 & j0.75 \end{bmatrix}$$

Now. $Z_b = j0.15$ between ② and ③.
Case 4:

$$j = 2$$

$$k = 3$$

$$\Rightarrow Z_{41} = Z_{21} - Z_{31} = j^{0.12}$$

$$Z_{42} = Z_{22} - Z_{32} = j^{0.92} - j^{0.6} = j^{0.32}$$

$$Z_{43} = -j^{0.15}$$

$$Z_{44} = Z_b + Z_{22} + Z_{33} - 2Z_{23}$$

$$= j^{0.15} + j^{0.92} + j^{0.75} - 2 * j^{0.6}$$

$$= j^{0.62}$$

$$\Rightarrow \left[\begin{array}{ccc|c} j0.72 & j0.72 & j0.6 & j^{0.12} \\ j0.72 & j0.92 & j0.6 & j^{0.32} \\ j0.6 & j0.6 & j0.75 & -j^{0.15} \\ \hline j0.12 & j0.32 & -j^{0.15} & j^{0.62} \end{array} \right] \Rightarrow$$

(150)

$$Z_{bus(\text{new})} \left\{ \right.$$

$$Z_{11} = j^{0.72} - \frac{j^{0.12} \times j^{0.12}}{j^{0.62}} = j^{0.6968}$$

$$Z_{12} = j^{0.658}$$

$$Z_{13} = j^{0.629}$$

$$Z_{bus(\text{new})} = \begin{bmatrix} j^{0.6968} & j^{0.6581} & j^{0.6290} \\ j^{0.6581} & j^{0.7548} & j^{0.6774} \\ j^{0.6290} & j^{0.6774} & j^{0.7132} \end{bmatrix}$$

11